

# VE270 Mid Exam Review

## Part 3: Combinational Circuit

Shi Li

2019.10.20

# Combinational Circuit compared with Sequential Circuit

- Truth table for a combinational circuit
- Output depends on input

p	q	$p \vee q$
T	T	T
T	F	T
F	T	T
F	F	F

- Characteristic table for a sequential circuit
- Output depends on input & previous state

S(t)	R(t)	Q(t)	Q(t+ $\Delta$ )	$\longrightarrow$ Q <sup>+</sup>
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	

# Design Process

- Capture the function
  - truth table/equation from requirements
- Convert to equation
  - k-map logic optimization
- Implement the circuit
  - from the optimized logic expression

# Design Process Exercise

## HW3 Problem 3

- Problem Description
- Input: 3 bits  $x_2x_1x_0$ , where  $x_0$  is the least significant bit (LSB).
- Output: 1 bit  $L$ , meaning low level of fuel.
- Specification: When the input is less than 3, the output is 1. Otherwise, the output is 0.



# Design Process Exercise

## HW3 Problem 3

- Step 1. Capture the function
  - $L = x_2'x_1'x_0' + x_2'x_1'x_0 + x_2'x_1x_0'$
- Step 2. Convert the equation
  - For simple equation, algebra method and k-map method are both useful.
  - However, for complicated equation, we prefer k-map method.
  - Here we use algebra method to simplify the expression for  $L$ .
  - $L = x_2'(x_1'x_0' + x_1'x_0 + x_1x_0') = x_2'(x_1x_0)'$
- Step 3. Implement the circuit



# How to draw the circuit elegantly?

## Good Examples

  



# How to draw the circuit elegantly?

## Better Examples

  

# How to draw the circuit elegantly?

## Bad Examples

  




# Combinational Building Blocks

## 1. MUX

 
- Example: 4 to 1 Mux
- Using 2 “switches” to choose one of the four input signals





- Question: If we have 35 input from  $i_0$  to  $i_{34}$ , how much “switches” do we need?
- Answer: 6 ( $i_{35} \sim i_{63}$  can be seen as don't cares)

# Combinational Building Blocks

## 2. Adder: Half Adder

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  

# Combinational Building Blocks

## 2. Adder: Full Adder

 


Q1: Which of the following gates CAN be placed here?

Q2: Which gate is the BEST choice to be placed here?

A. AND      B. OR      C. XOR      D. NAND

# Combinational Building Blocks

## 2. Adder: Full Adder

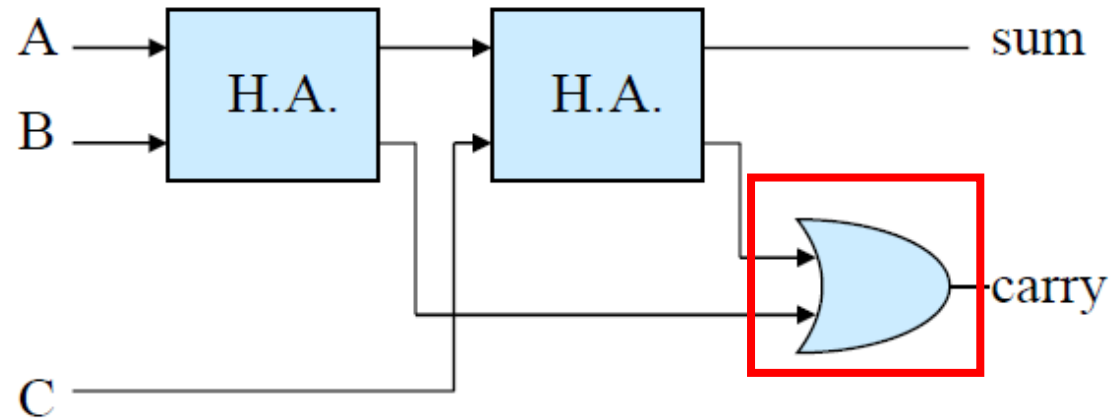

Q1: OR, XOR


Q2: OR is the best.

(4 transistors for OR gate, at least 6 transistors for XOR gate)

# Combinational Building Blocks
 
## 2. Adder: Carry-Ripple Adder


- For a carry-ripple adder with 4-bit input, it generates 5-bit output.



# Combinational Building Blocks

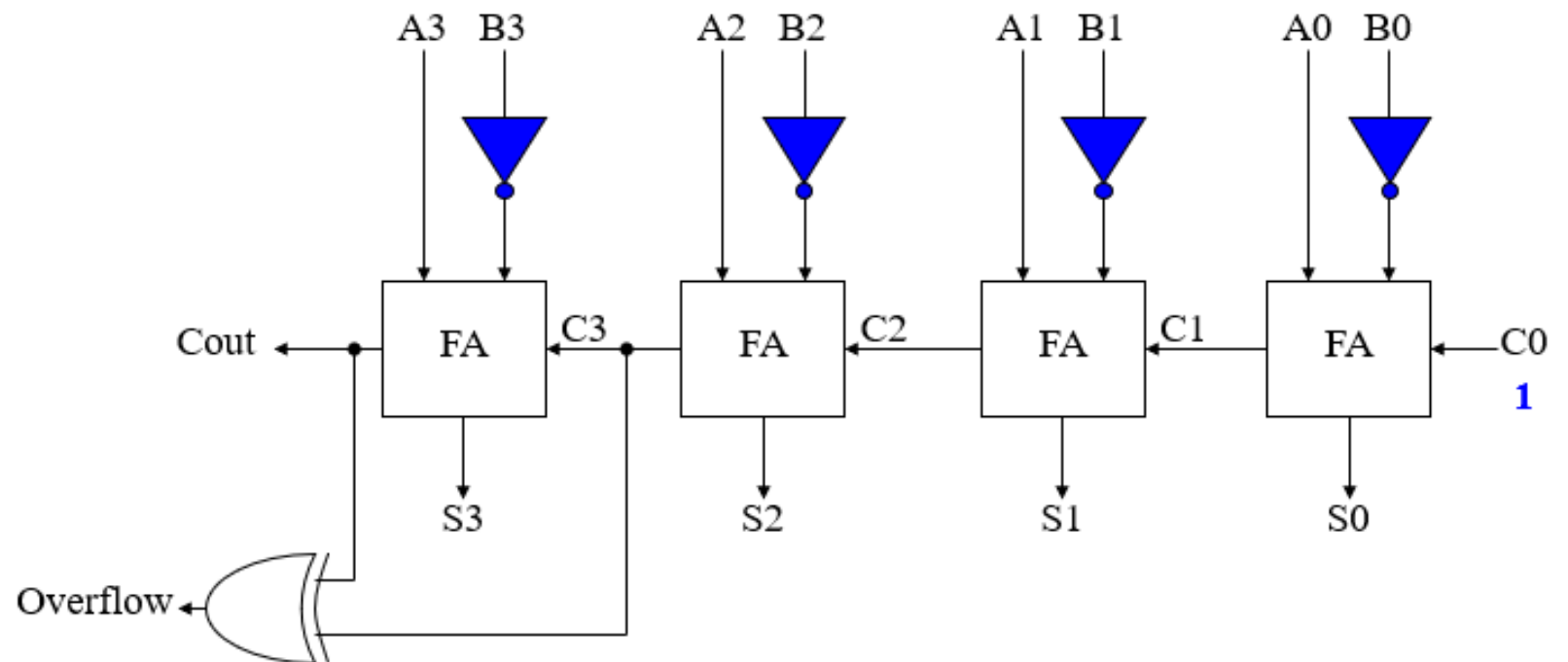
## 2. Adder: Subtractor (for 2's complement numbers)

- When we do subtraction, we need to
- 1. add inverters to B input
- 2. set C0 to 1



# Combinational Building Blocks

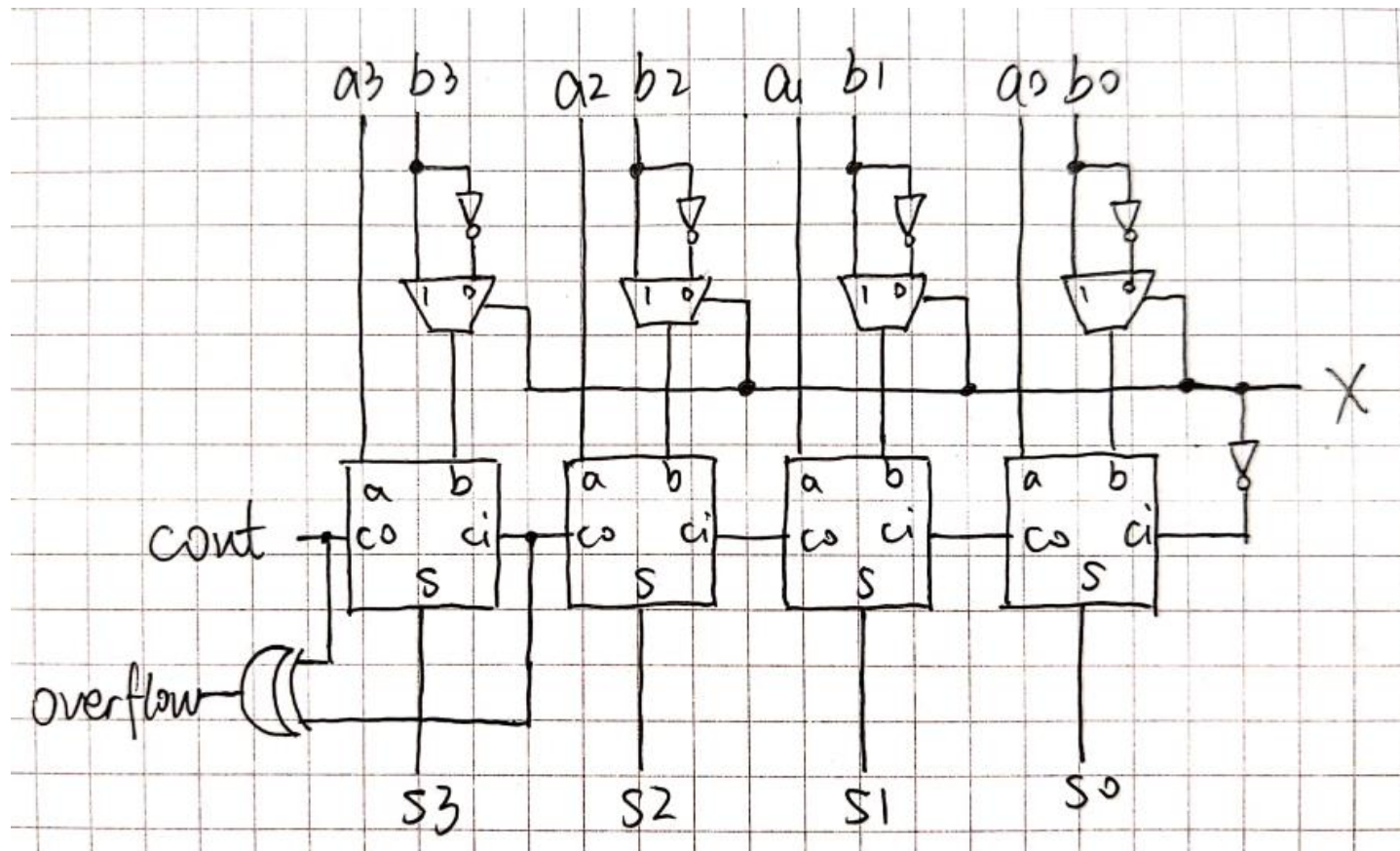- Exercise: Add a switch to choose “add” mode or “subtract” mode



# Combinational Building Blocks

## 3. Encoder & Decoder

Inputs								Outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1



Inputs			Outputs							
x	y	z	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



# Combinational Building Blocks
  
## 3. Encoder & Decoder



- Decoder:  $N$  inputs,  $2^N$  outputs
- Enable  $e$  (Question: How to implement it in the circuit?)
- Use decoder to implement any combinational circuit



# Combinational Building Blocks
  
## 3. Encoder & Decoder


- Decoder:  $N$  inputs,  $2^N$  outputs
- Enable  $e$  (Question: How to implement it in the circuit? – Red lines)
- Use decoder to implement any combinational circuit




# Combinational Building Blocks
 
## 4. Buffer & Tri-state Buffer


- Why we use buffers?
  - Amplify the driving capability of a signal
  - Insert delay
  - Protect input from output
- Why we use tri-state buffer?
  - Provide another state “Z”
  - Z: high impedance



B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

 

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

 

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z

Use the 60 questions to help you review.

## **60 Questions for VE270 Midterm Exam Review**

### **VE270 2019 Fall TA Group**

1. How do digital signals and analog signals look like?
2. How to convert binary numbers to decimal numbers?  
Example:  $(1101.011)_2 = ( \quad )_{10}$
3. What are the two methods to convert decimal numbers to binary numbers?  
Example:  $(19.25)_{10} = ( \quad )_2$
4. How to convert among binary numbers, octal numbers, and hexadecimal numbers?
5. How to convert base-m numbers to base-n numbers?