

Midterm [Part 2]

2019.10.20.

Hao Zhiyu

Outline

1. Logic circuit
2. Optimization

Theorems

- | | | |
|-------------------------------------|-----------------------------|----------------|
| • (a) $x + 0 = x$; | (b) $x \cdot 0 = 0$; | (theorem 1) |
| • (a) $x + x' = 1$; | (b) $x \cdot x' = 0$; | (theorem 2) |
| • (a) $x + x = x$; | (b) $x \cdot x = x$; | (theorem 3) |
| • (a) $x + 1 = 1$; | (b) $x \cdot 1 = x$; | (theorem 4) |
| • $(x')' = x$; | | (involution) |
| • (a) $x + y = y + x$; | (b) $xy = yx$; | (commutative) |
| • (a) $x + (y + z) = (x + y) + z$; | (b) $x(yz) = (xy)z$; | (associative) |
| • (a) $x(y + z) = xy + xz$; | (b) $x + yz = (x+y)(x+z)$; | (distributive) |
| • (a) $x + xy = x$; | (b) $x(x + y) = x$; | (absorption) |
| • (a) $xy + xy' = x$; | (b) $(x + y)(x + y') = x$ | (theorem 5) |
| • (a) $x + x'y = x + y$ | (b) $x(x' + y) = xy$ | (theorem 6) |

Hw2

9. Problem 6.4, using both algebraic methods and K-map. (10 points)

6.4 Perform two-level logic size optimization for $F(a, b, c) = a + a'b'c + a'c$ using a K-map.

$$F(a,b,c) = a + a'c = a + ac + a'c = a + (a+a')c = a + c.$$

Read through the question carefully!!!

Boolean Algebra

- De Morgan's Law
- Minterm and Maxterm

			Minterms		Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x+y+z$	M_0
0	0	1	$x'y'z$	m_1	$x+y+z'$	M_1
0	1	0	$x'yz'$	m_2	$x+y'+z$	M_2
0	1	1	$x'yz$	m_3	$x+y'+z'$	M_3
1	0	0	$xy'z'$	m_4	$x'+y+z$	M_4
1	0	1	$xy'z$	m_5	$x'+y+z'$	M_5
1	1	0	xyz'	m_6	$x'+y'+z$	M_6
1	1	1	xyz	m_7	$x'+y'+z'$	M_7

$$(a) (x + y)' = x'y'$$

$$(b) (xy)' = x' + y'$$

For the final result, it is better to simplify the answer.

Find Expression

- First to minterms
- Know how to transfer to maxterms
- Don't Care Situation

<u>Truth Table</u>			
x	y	z	F1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Sum-of-minterms

$$F1 = x'y'z + xy'z' + xy'z + xyz' + xyz$$

$$F1 = m_1 + m_4 + m_5 + m_6 + m_7$$

$$F1 = \Sigma (1, 4, 5, 6, 7)$$

Product-of-maxterms


$$F1 = (x+y+z) \cdot (x+y'+z) \cdot (x+y'+z')$$

$$F1 = M_0 \cdot M_2 \cdot M_3$$


$$F1 = \Pi (0, 2, 3)$$

Logic gates

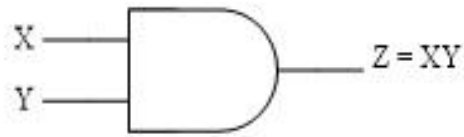
- 1 gate 1 delay (inverter ignored, XOR treated as usual)
- 2 transistors (size) for each gate input



2-input AND gate

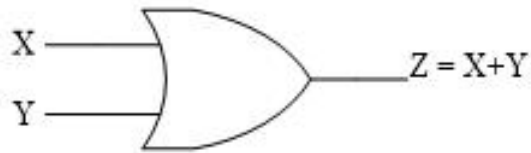

2-input OR gate

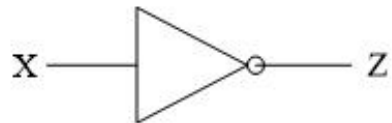


NOT gate/Inverter



NAND			NOR			XOR			XNOR		
x	y	F	x	y	F	x	y	F	x	y	F
0	0	1	0	0	1	0	0	0	0	0	1
0	1	1	0	1	0	1	0	1	0	1	0
1	0	1	1	0	0	1	0	1	1	0	0
1	1	0	1	1	0	1	1	0	1	1	1

- NAND: Opposite of AND (“NOT AND”)
- NOR: Opposite of OR (“NOT OR”)
- XOR: outputs 1 when inputs have odd number of 1’s
- XNOR: Opposite of XOR (“NOT XOR”)

Hw3

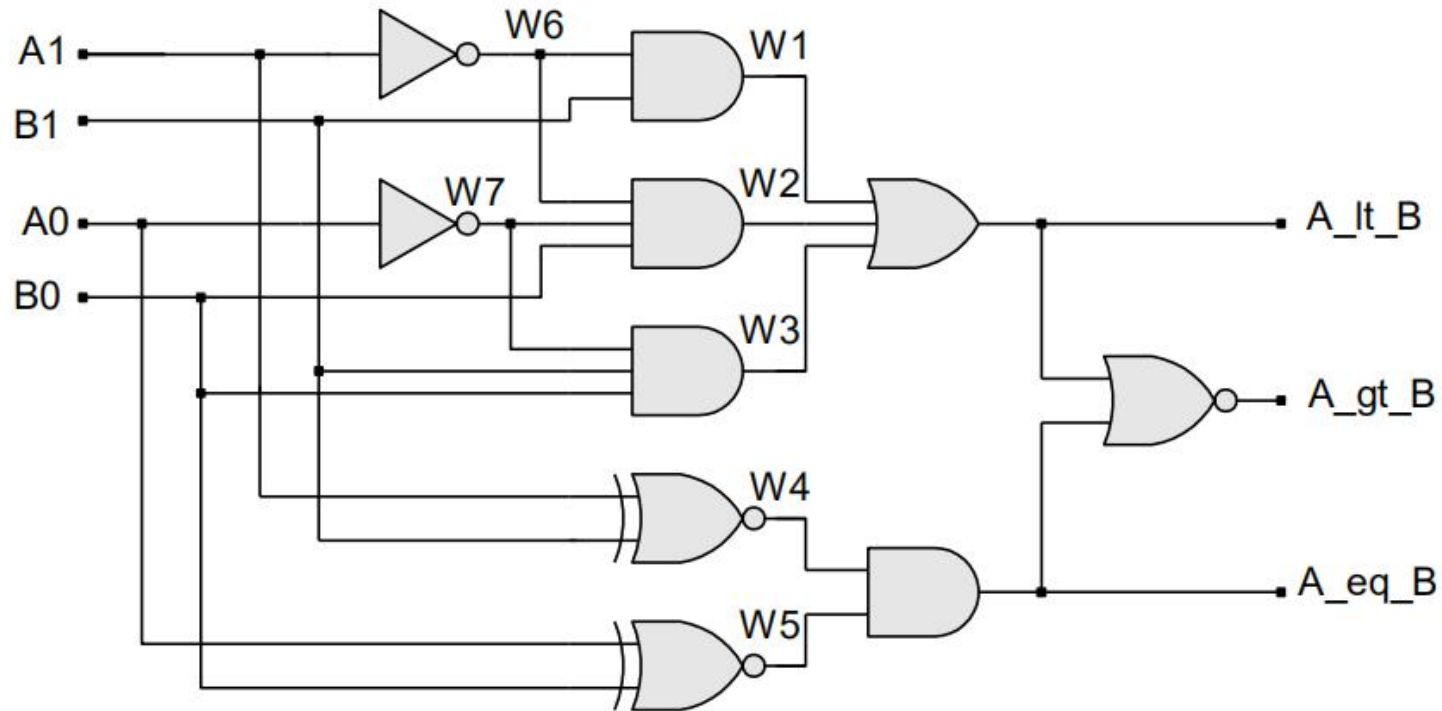10. Highlight the critical paths of the following circuit. Assume that each gate (including the individual inverters and XOR gates) has a delay of 1 ns and each wire has a delay of 0.5 ns.
(5 points)



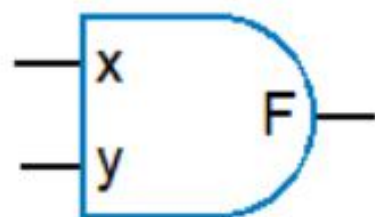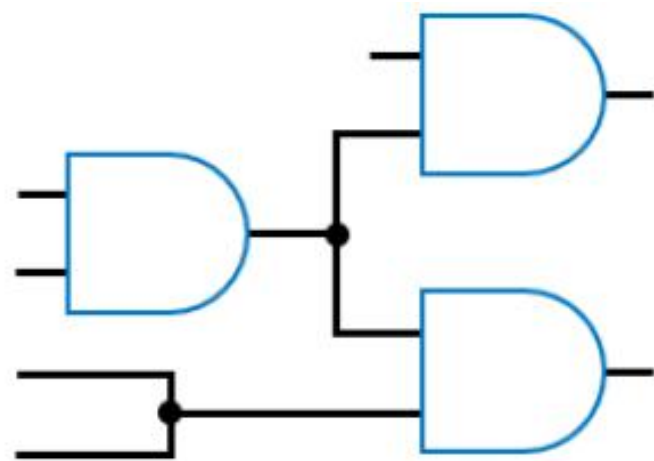

K-map

- Building from truth table
- Grouping
- Find Pls and EPls
- Practice makes perfect!!!

Building

- From truth table
- From current equation (first transfer to truth table)

W	X	Y	Z	F		
0	0	0	0	1	m0	$W'X'Y'Z'$
0	0	0	1	0	m1	$W'X'Y'Z$
0	0	1	0	1	m2	$W'X'YZ'$
0	0	1	1	1	m3	$W'X'YZ$
0	1	0	0	0	m4	$W'XY'Z'$
0	1	0	1	0	m5	$W'XY'Z$
0	1	1	0	0	m6	$W'XYZ'$
0	1	1	1	1	m7	$W'XYZ$
1	0	0	0	1	M8	$WX'Y'Z'$
1	0	0	1	1	m9	$WX'Y'Z$
1	0	1	0	0	M10	$WX'YZ'$
1	0	1	1	0	m11	$WX'YZ$
1	1	0	0	1	m12	$WXY'Z'$
1	1	0	1	0	m13	$WXY'Z$
1	1	1	0	0	m14	$WXYZ'$
1	1	1	1	1	m15	$WXYZ$

		YZ			
		00	01	11	10
WX	Y'Z'	Y'Z	YZ	YZ'	
W'X'	1 m0	0 m1	1 m3	1 m2	
W'X	0 m4	0 m5	1 m7	0 m6	
WX	1 m12	0 m13	1 m15	0 m14	
WX'	1 m8	1 m9	0 m11	0 m10	

PI and EPI

- A prime implicant (PI) is a group that cannot be **entirely** contained by another implicant
- A prime implicant (PI) is essential if **one** of its cells is covered **ONLY** by that PI

F		YZ			
WX		00	01	11	10
	00	1	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

— Prime implicant
..... Not prime implicant

F		YZ			
WX		00	01	11	10
	00	1	0	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	1

Essential PI: XZ

F		YZ			
WX		00	01	11	10
	00	1	0	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	1

No essential PIs found