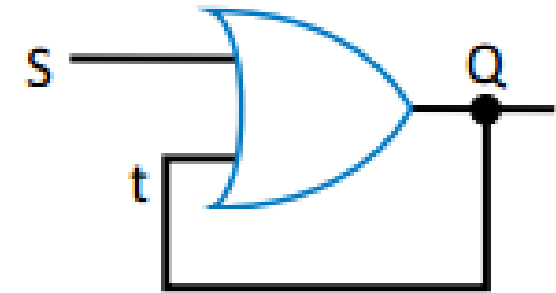


# Latch & Flip flop

# Sequential Circuit

- Output depends on both present inputs and history of inputs and outputs.
- It is combinational circuit with feedback




# Latch & Flip-flop

- Building blocks that can store value of a bit
- Latch is level sensitive
- Flip-flop is edge sensitive

# SR Latch

- $S=1$ : set  $Q$  to 1
- $R=1$ : reset  $Q$  to 0


$S(t)$	$R(t)$	$Q(t)$	$Q(t+\Delta) \rightarrow Q^+$	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	

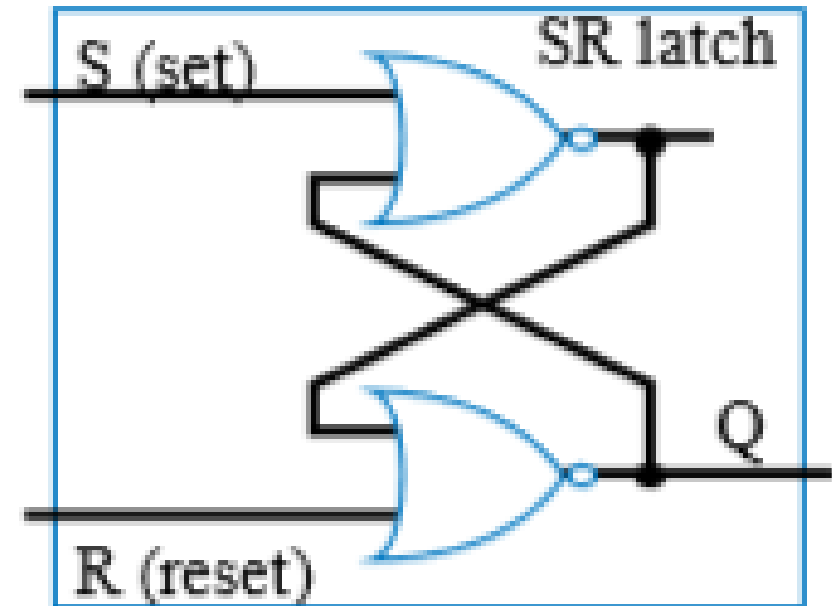


$$Q^+ = S + R'Q$$
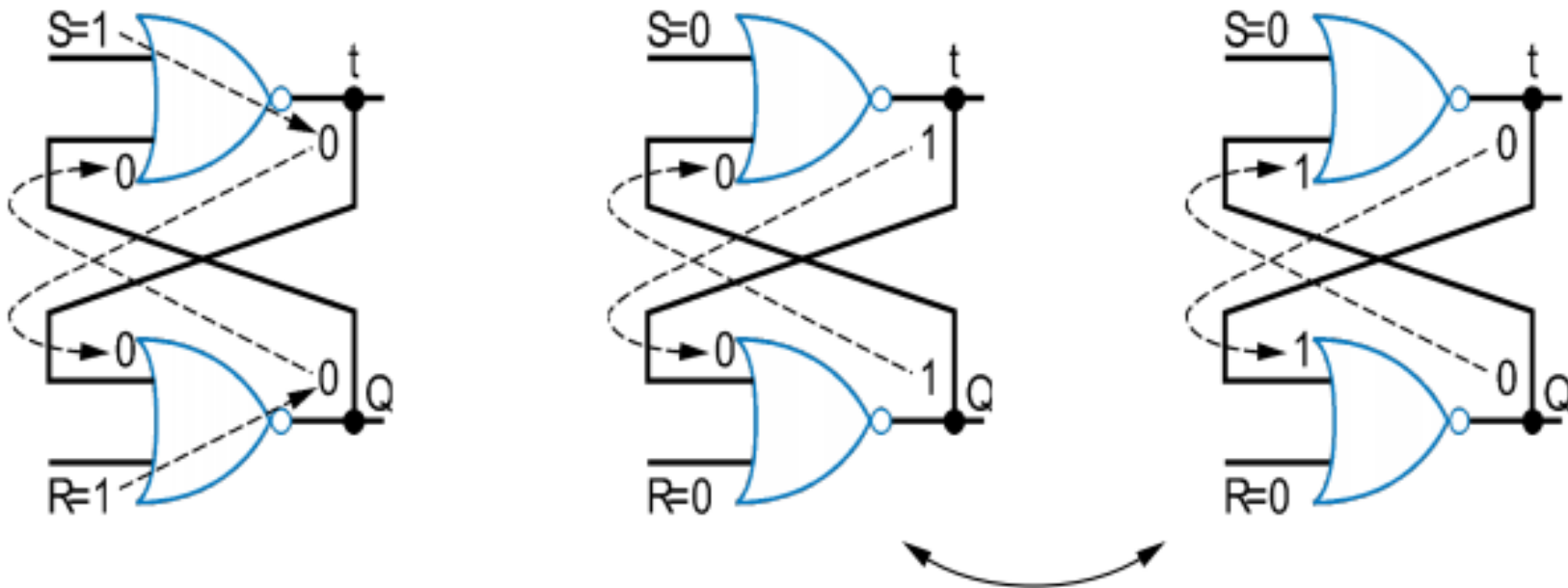
# SR Latch

- When  $S=1$  &  $R=1$ ,  $Q$  may oscillate when they both return to 0 simultaneously.



# Gated SR Latch

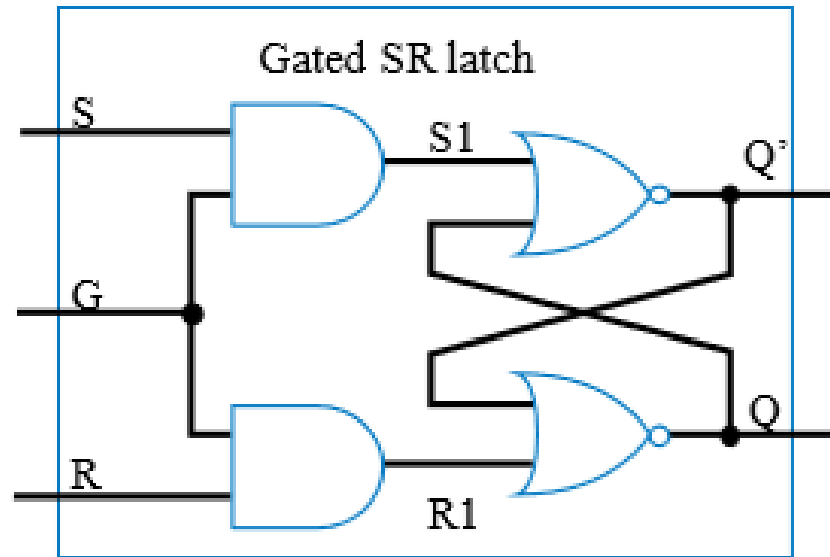


Characteristic Table


G	S	R	Q <sup>+</sup>
0	x	x	Q; Latch locked
1	0	0	Q; Hold state
1	0	1	0; Reset state
1	1	0	1; Set state
1	1	1	not allowed
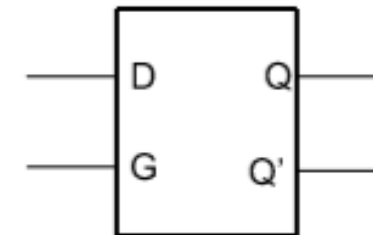
# Gated D Latch

- No unstable state as in SR latch
- $Q = D$  when  $G = 1$
- $Q$  holds when  $G = 0$



D latch  
symbol

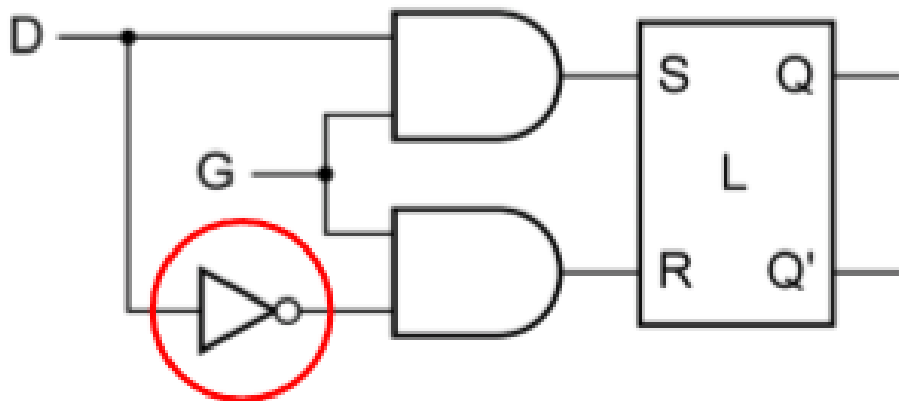


Characteristic Table

G	D	Q <sup>+</sup>
1	0	0
1	1	1
0	X	Q
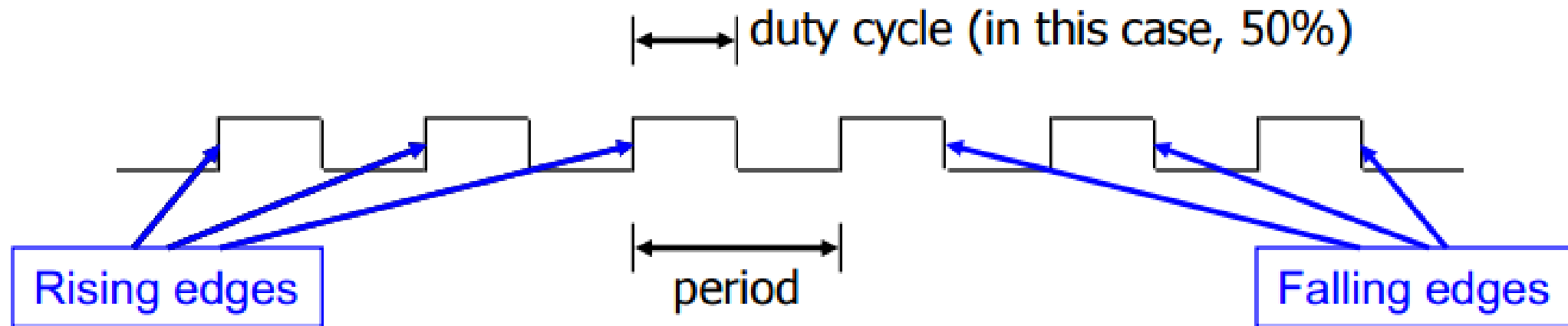
# Clock Signal



- Periodic pulse train
- Clock period: time interval between pulses





# Rising-Edge Triggered D Flip Flop


- Edge sensitive

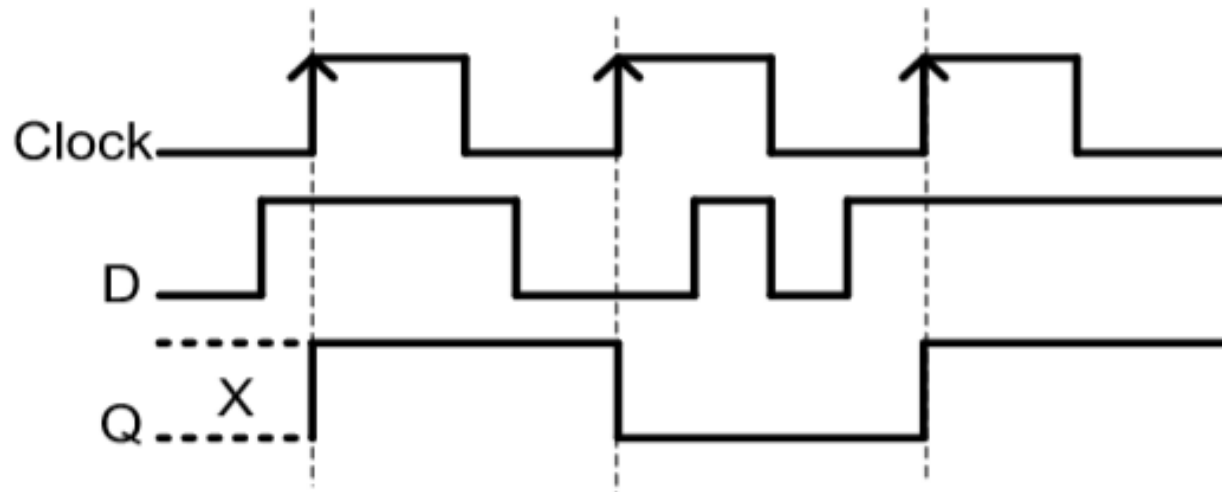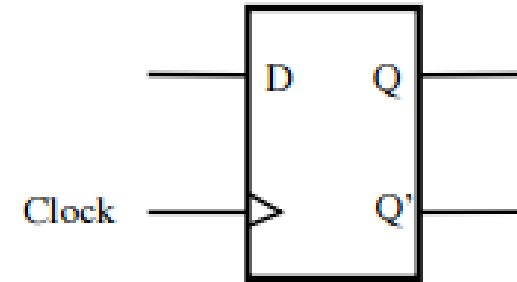

clock	D	Q <sup>+</sup>
	0	0
	1	1
0	X	Q
1	X	Q

Characteristic equation:  
 $Q^+ = D$  (at active clock edges)


# Rising-Edge Triggered J-K Flip Flop

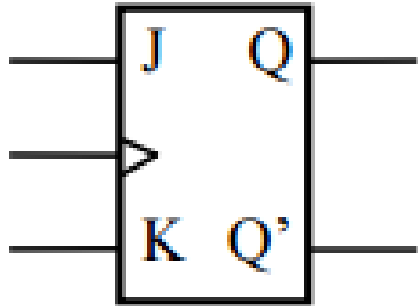

J	K	Q <sup>+</sup>
0	0	Q
0	1	0
1	0	1
1	1	Q'

Characteristic equation:  
 $Q^+ = JQ' + K'Q$

# Rising-Edge Triggered T Flip Flop


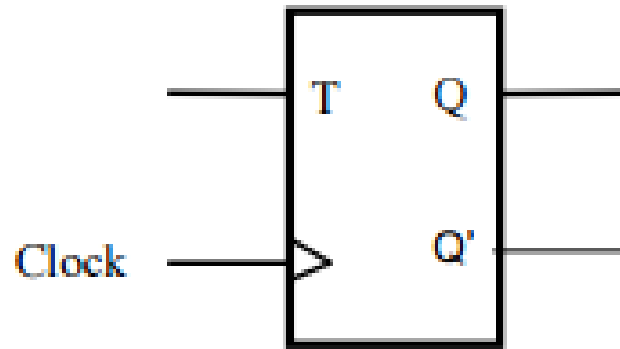


clock	T	Q <sup>+</sup>
	0	Q
	1	Q'

Characteristic equation:  
 $Q^+ = T'Q + TQ' = T \oplus Q$
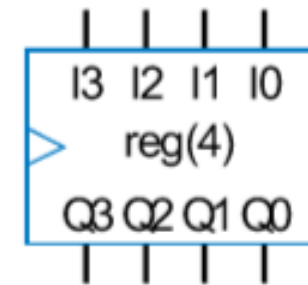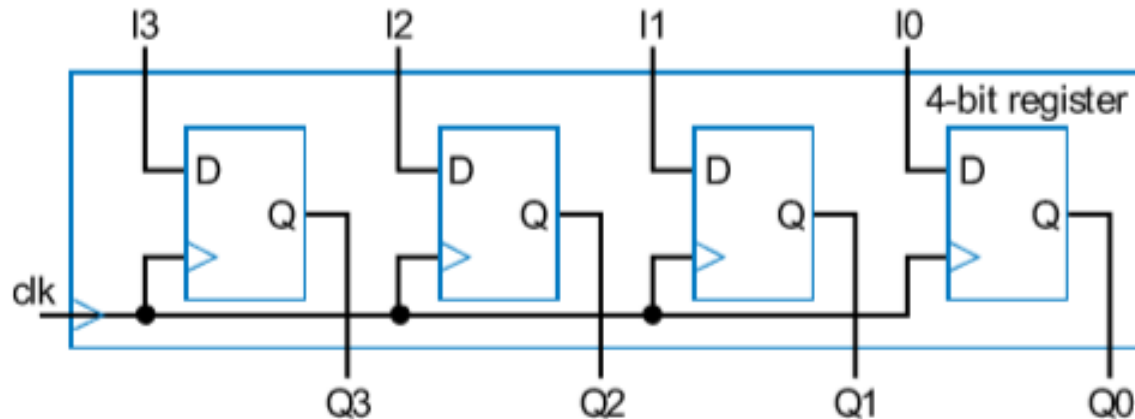
# Register



- Multiple flip-flops sharing clock signal
- Store multiple bits
- Load values simultaneously at rising edge





# Control Inputs for Flip Flops

- Synchronous/asynchronous: depends on the clock signal or not
- Active low/high: controls when it's low/high
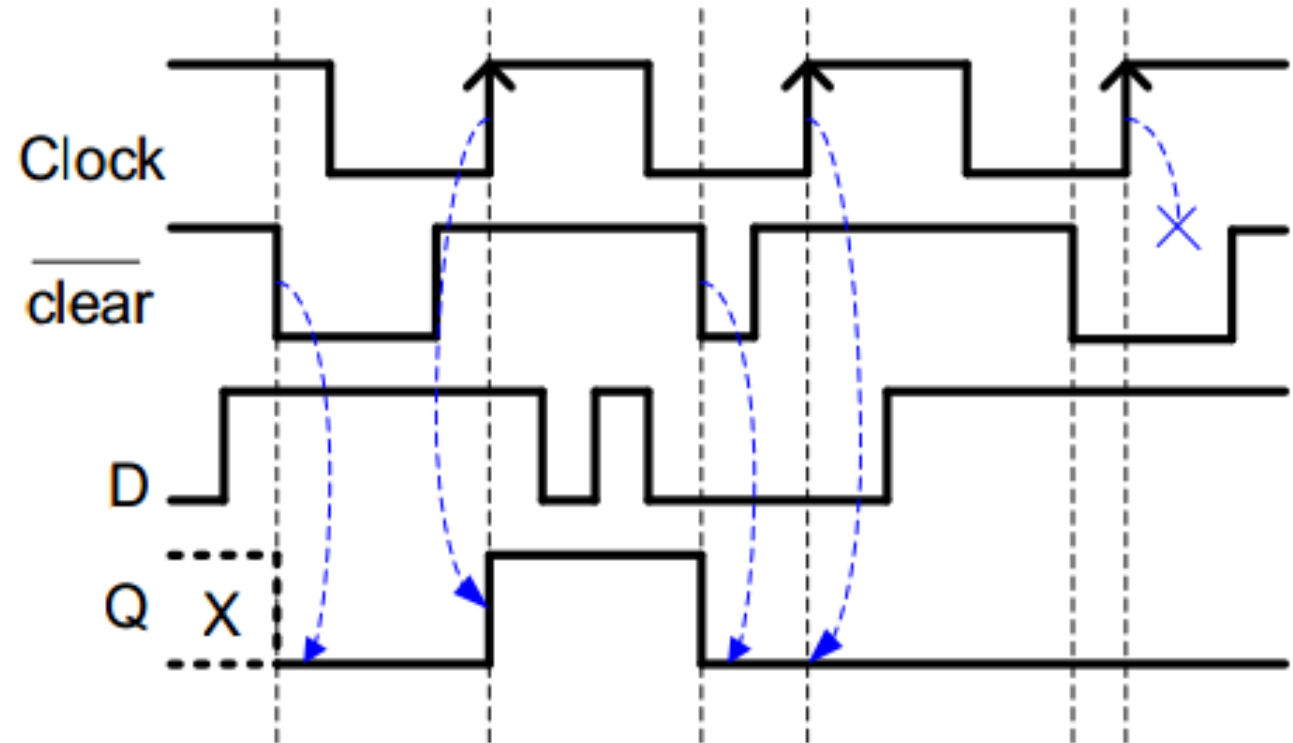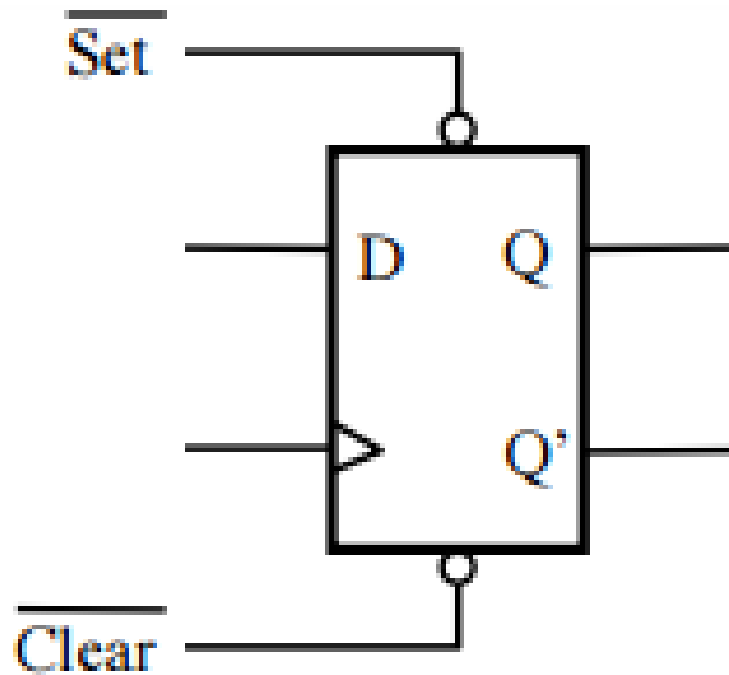
# D flip flop with active low asynchronous Clear


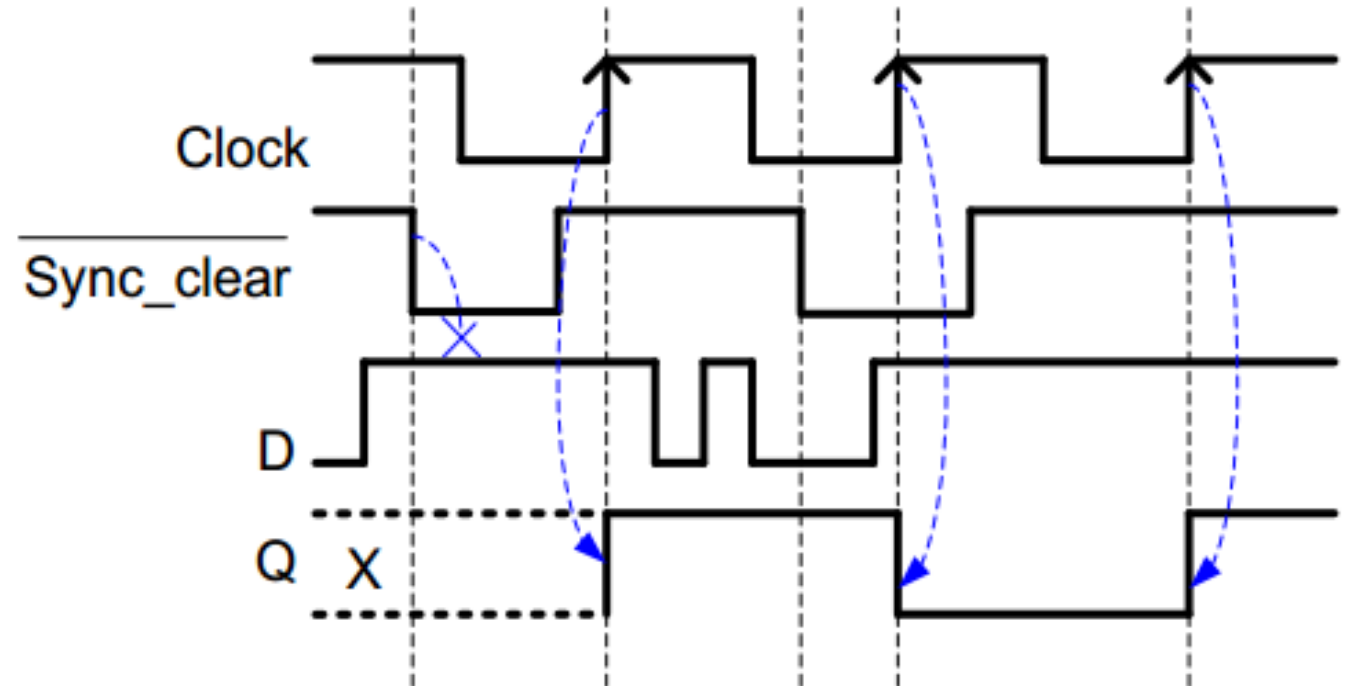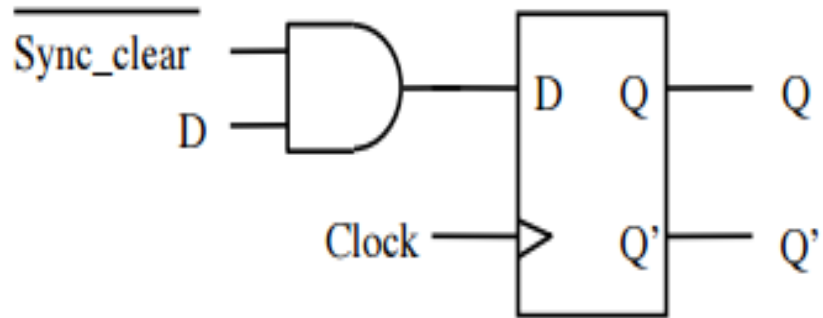
# D flip flop with active low synchronous Clear



Verilog



# Verilog HDL


## Syntax:

- module
- always
- if...else...
- switch
- assignment

## Tips:

- [N-1:0] represents N bits
- Destination variables inside *always* must be *reg* type

# Module

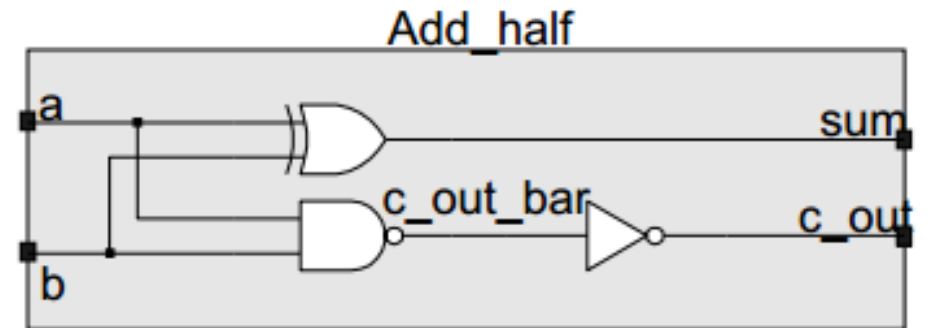

```
module Add_half (sum, c_out, a, b);  
  input  a, b;  
  output sum, c_out;  ← declaration of port modes  
  
  wire c_out_bar; ← declaration of internal signal  
  
  xor (sum, a, b);  
  nand (c_out_bar, a, b);  
  not (c_out, c_out_bar);  
endmodule
```

← instantiation of pre-defined primitive gates


Same variable indicates connection

# Module

```
module Add_full (sum, c_out, a, b, c_in); // parent module
  input    a, b, c_in;
  output   c_out, sum;
  wire     w1, w2, w3;


  Add_half M1 (w1, w2, a, b);           // child module
  Add_half M2 (sum, w3, w1, c_in);      // child module
  or (c_out, w2, w3);                   // primitive instantiation
endmodule
```

Module instance name

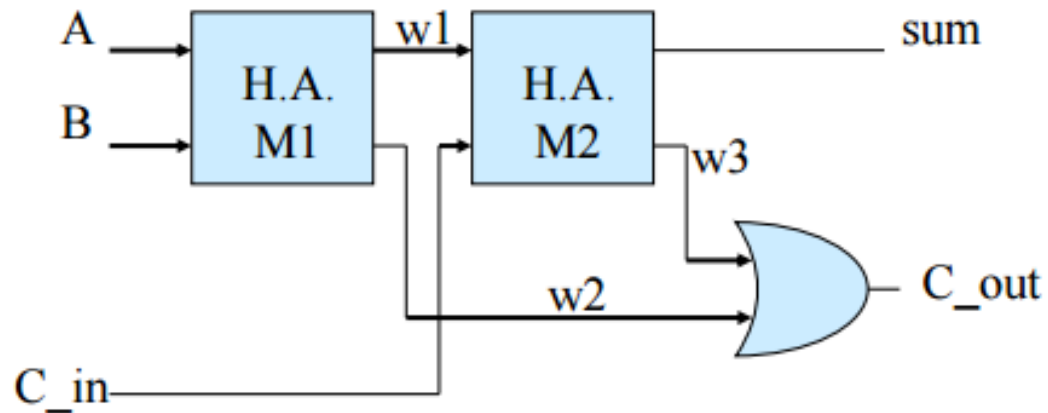

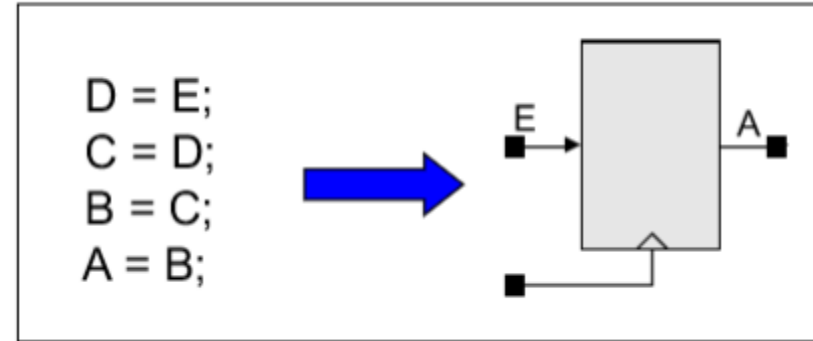
# Assignment

- =  
Assign one statement by one statement



- <=  
Assign simultaneously

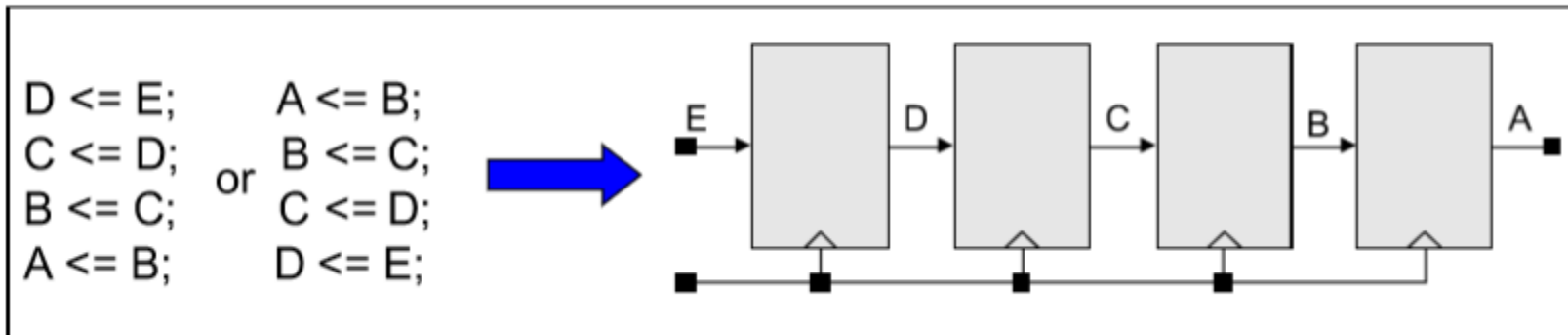

# Testbench

Outputs of the module

Inputs of the module

Module to be tested

Changes of inputs

```
module Test_Banch;
    parameter half_period = 50;
    parameter counter_size = 4;

    wire [counter_size-1:0] Q;
    reg [counter_size-1:0] Din;
    reg clock, load, reset, CE;

    counter_N_bit #(counter_size) UUT (clock,reset,load,CE,Din,Q,CEO);

    initial begin
        #0      clock = 0; Din = 0; load = 0; CE = 1; reset = 1;
        #100    reset = 0;
        #200    Din = 8; load = 1;
        #100    load = 0;
        #300    CE = 0;
        #200    CE = 1;
    end



    always #half_period clock = ~clock;

    initial #2000 $stop;
endmodule
```


Counter
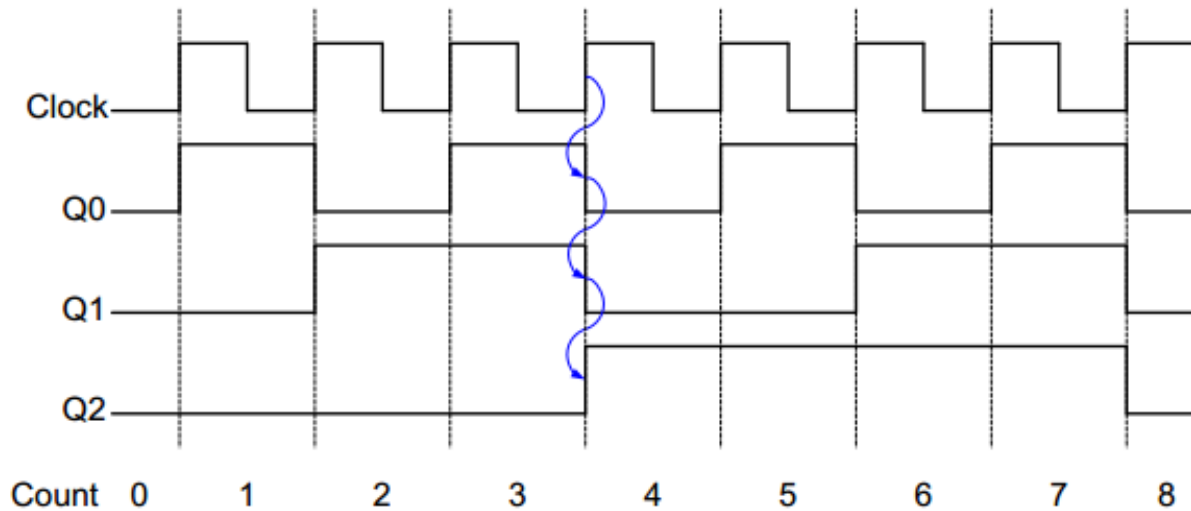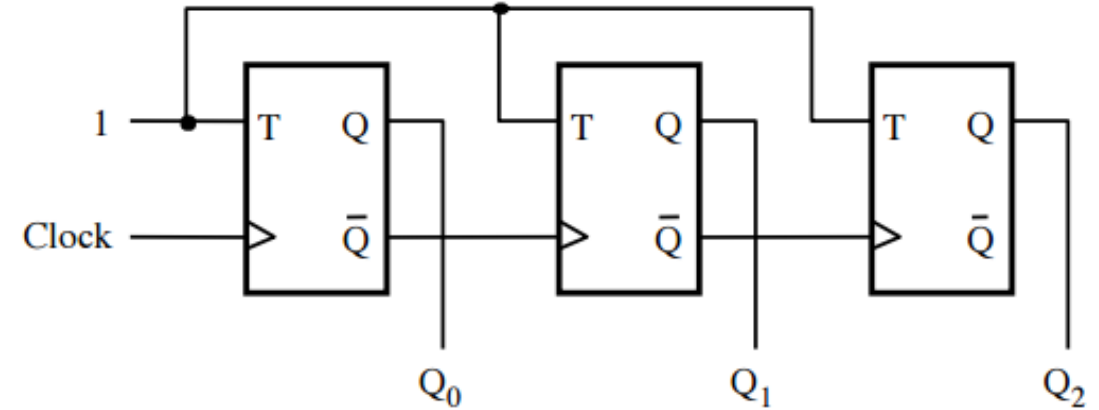
# Asynchronous Counter

- Flip flops are cascaded together
- Delays  $\rightarrow$  asynchronous output



Ideal

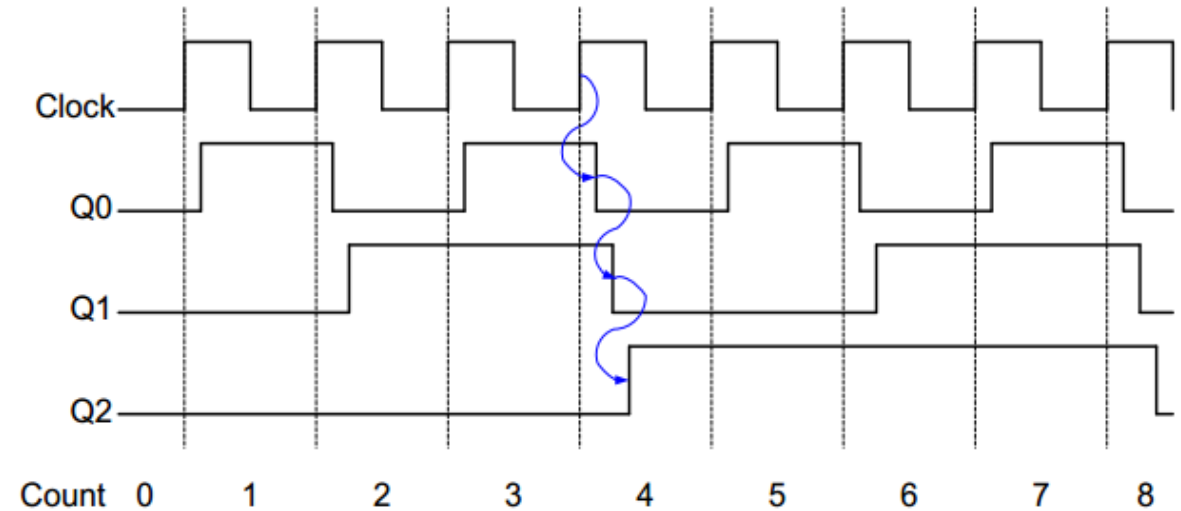


Practical

# Synchronous Counter

- All the flip-flops are triggered by the same clock
- May be implemented by different type of flip flops



## Synchronous 3-bit Binary Counter

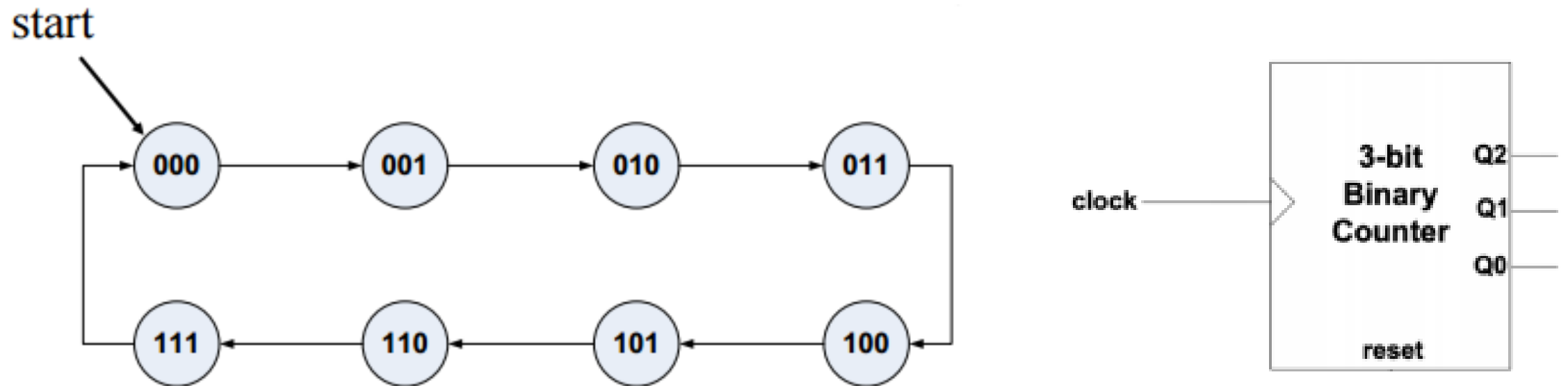



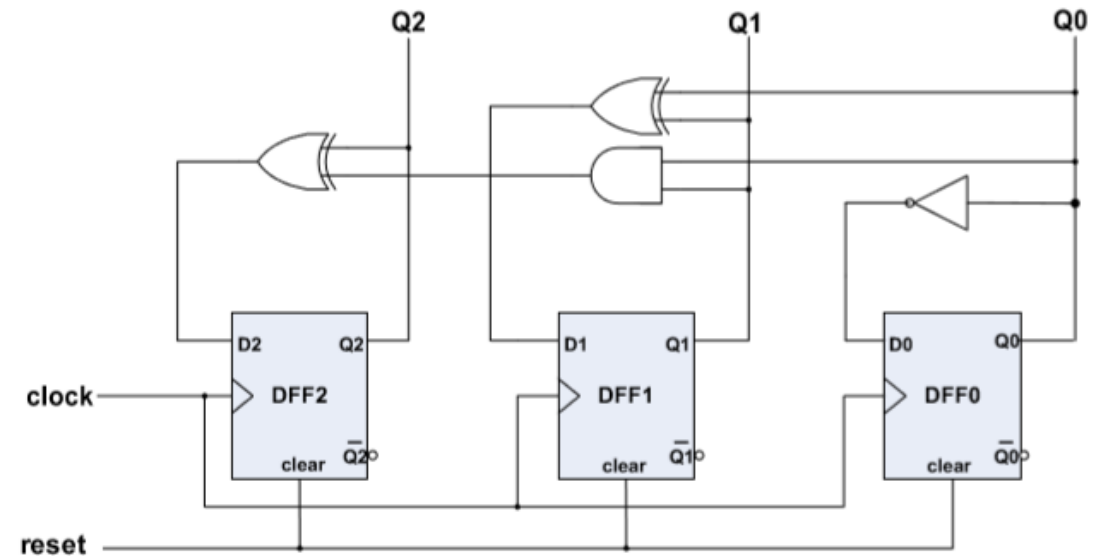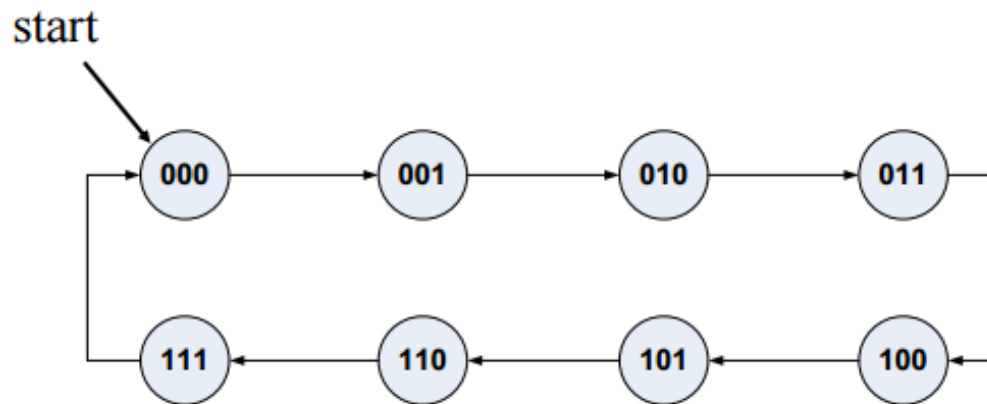
# How to design a synchronous counter given a sequence of numbers?

- Combine combinational circuit and sequential circuit
- Steps:
  1. Decide what kinds of flip flops to use and how many
  2. Draw truth table
  3. Derive logic equations
  4. Draw combinational circuit



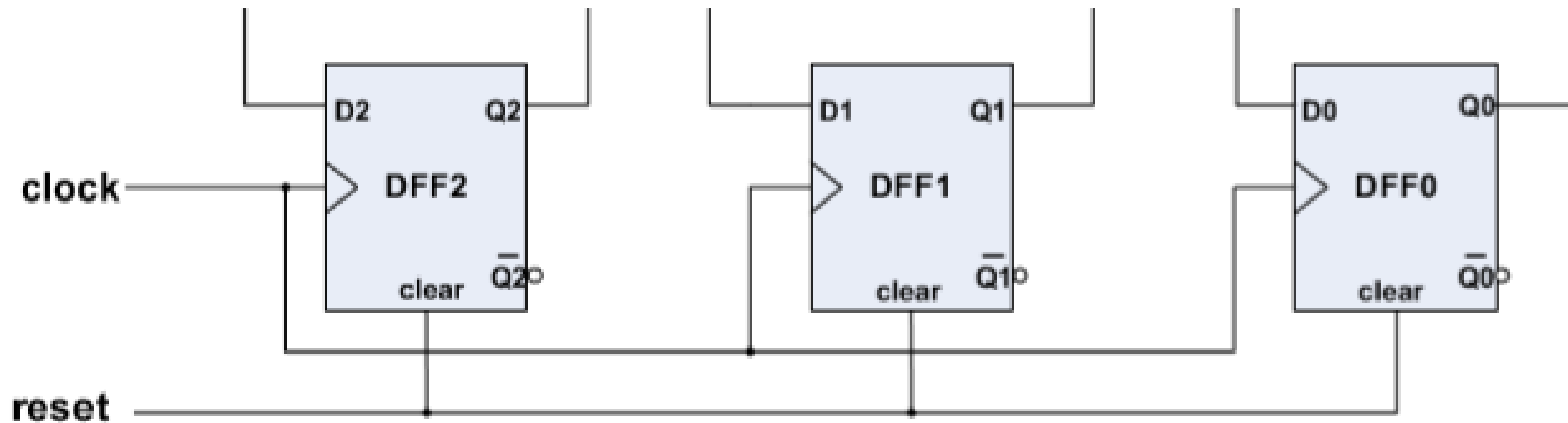
## Step 1: FF

- 3-bit counter  $\rightarrow$  3 flip flops
- Here we choose D flip flops



## Step 2: Draw Truth Table

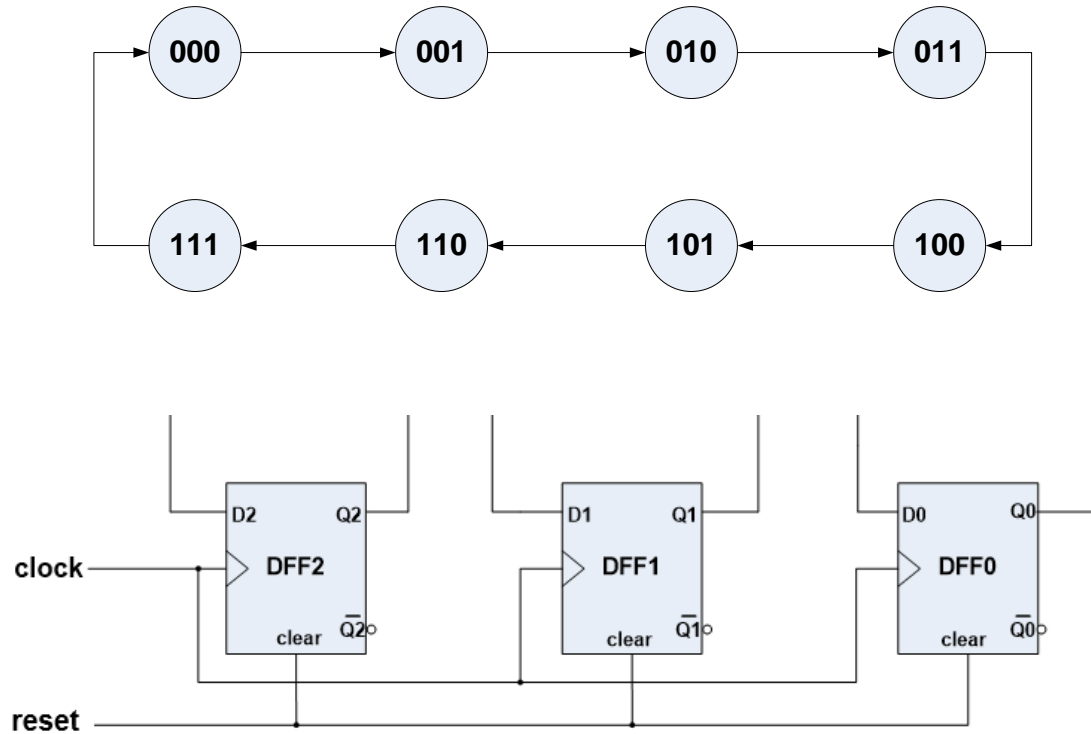

$Q^+ = D$  upon active edge

Present State			Next State			D flip flop input		
Q2	Q1	Q0	Q2 <sup>+</sup>	Q1 <sup>+</sup>	Q0 <sup>+</sup>	D2	D1	D0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

## Step 3: Derive Logic Equations

Present State			Next State			D flip flop input		
Q2	Q1	Q0	Q2 <sup>+</sup>	Q1 <sup>+</sup>	Q0 <sup>+</sup>	D2	D1	D0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

$$\begin{aligned}
 D2 &= Q2Q1' + Q2Q0' + Q2'Q1Q0 \\
 &= Q2(Q1' + Q0') + Q2'Q1Q0 \\
 &= Q2(Q1Q0)' + Q2'(Q1Q0) \\
 &= Q2 \oplus (Q1Q0)
 \end{aligned}$$

$$\begin{aligned}
 D1 &= Q1'Q0 + Q1Q0' \\
 &= Q1 \oplus Q0
 \end{aligned}$$


$$D0 = Q0'$$

## Step 3: Draw Combinational Circuit

$$\begin{aligned} D2 &= Q2Q1' + Q2Q0' + Q2'Q1Q0 \\ &= Q2(Q1' + Q0') + Q2'Q1Q0 \\ &= Q2(Q1Q0)' + Q2'(Q1Q0) \\ &= Q2 \oplus (Q1Q0) \end{aligned}$$

$$\begin{aligned} D1 &= Q1'Q0 + Q1Q0' \\ &= Q1 \oplus Q0 \end{aligned}$$

$$D0 = Q0'$$

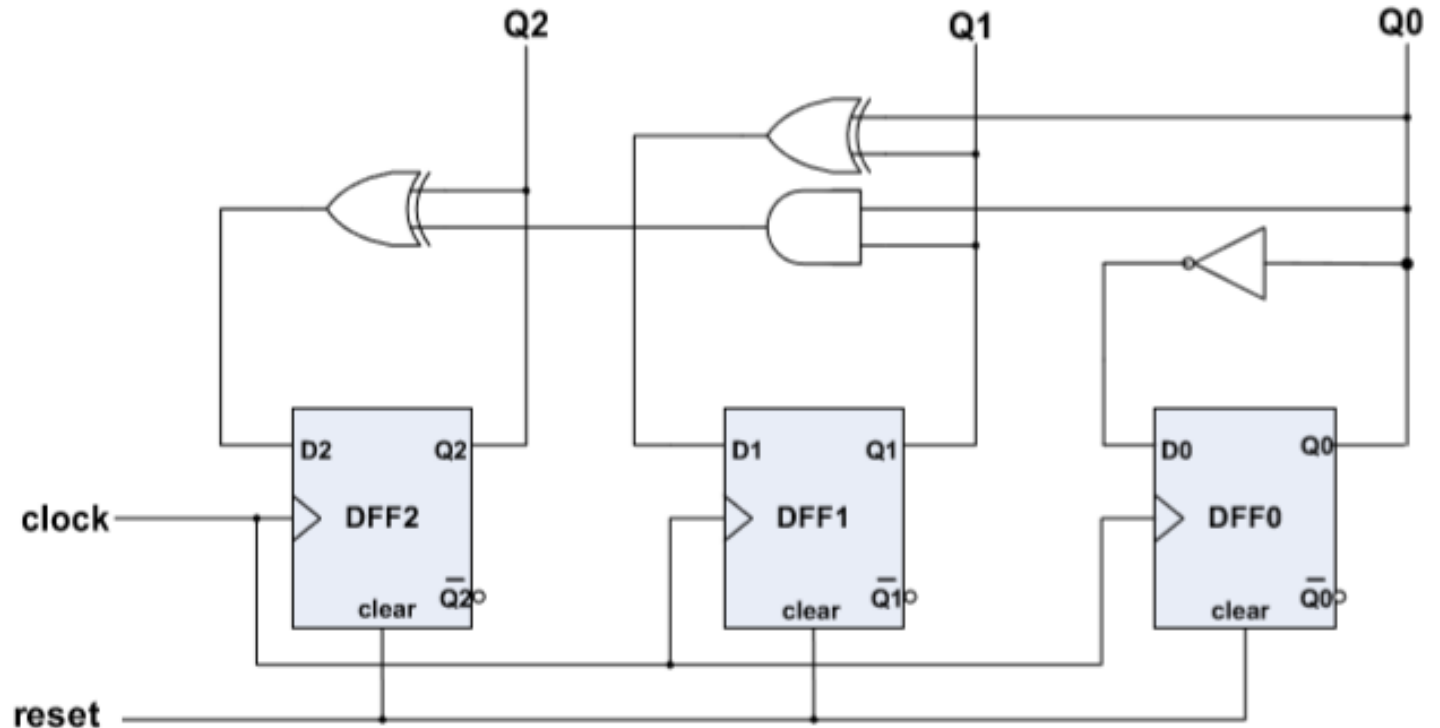


# Control Signals

Priority of External Control Signals:

reset	load	CE	Action on the rising clock edge
1	X	X	Clear ( $Q_n \leq 0$ )
0	1	X	Load ( $Q_n \leq D_n$ )
0	0	1	Count
0	0	0	Hold (No Change)

Count Enable Output:
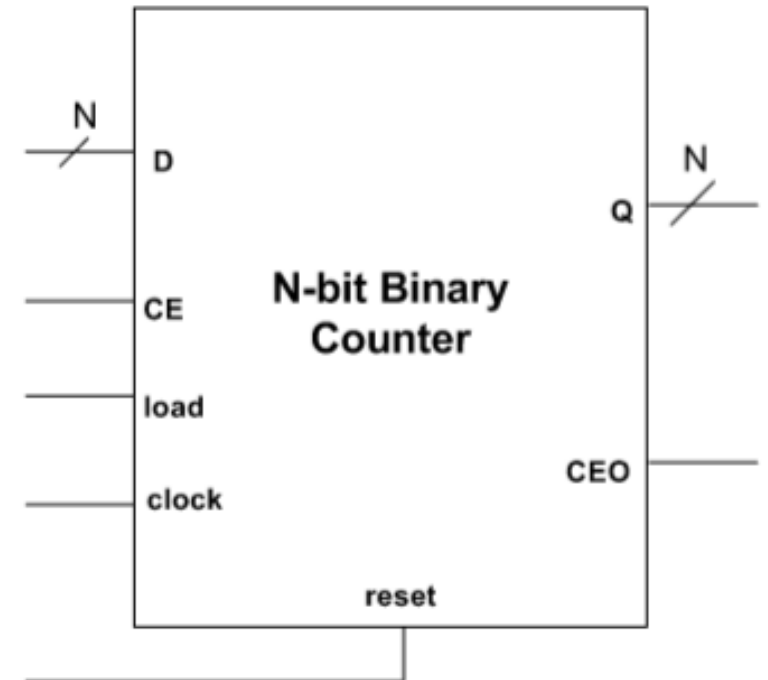
$$CEO = CE \cdot Q_{N-1} \cdot Q_{N-2} \cdot \dots \cdot Q_0$$




# Clock Divider

Divide by N:

- $2^{n-1} < N < 2^n$ ,  
where n is the size  
of counter
- N-1 is the upper  
bound of the  
counter's sequence
- AND the bits that  
are 1 in the upper  
bound to the load

Divide by 6:

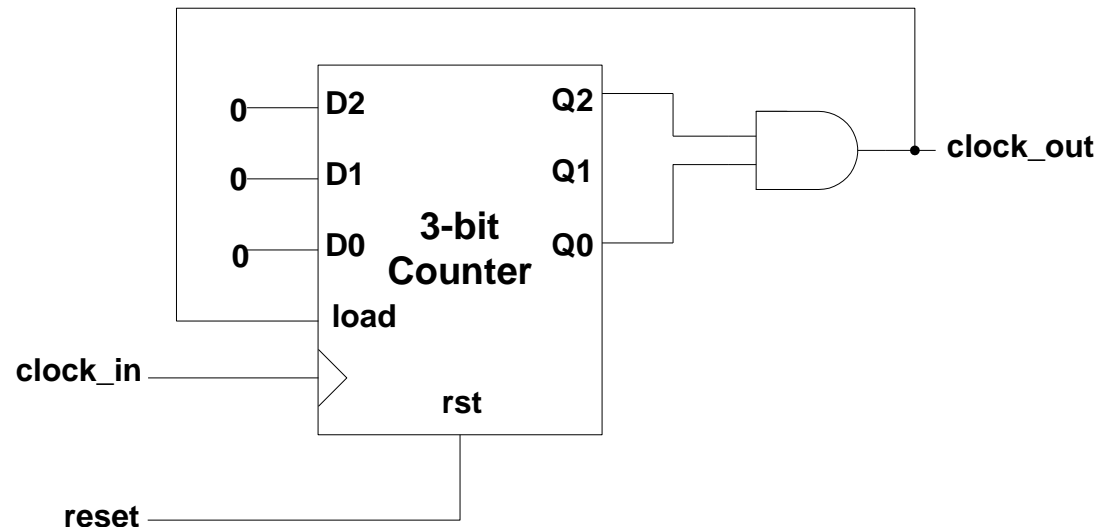- $2^2 < 6 < 2^3 \rightarrow$  3-bit counter
- Countering sequence:  
 $000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 000$
- Upper bound:  $101 \rightarrow \text{load} = Q0 \text{ AND } Q2$



GOOD LUCK